 


# RISC-V *CPU Datapath, Control Intro*

# Design Principles

- Five steps to design a processor:

- 1) Analyze instruction set → datapath requirements
- 2) Select set of datapath components & establish clock methodology
- 3) Assemble datapath meeting the requirements
- 4) Analyze implementation of each instruction to determine setting of control points that effects the register transfer
- 5) Assemble the control logic
  - Formulate Logic Equations
  - Design Circuits



# Summary !

- Universal datapath
  - Capable of executing all RISC-V instructions in one cycle each
  - Not all units (hardware) used by all instructions
- 5 Phases of execution
  - IF (Instruction Fetch), ID (Instruction Decode), EX (Execute), MEM (Memory), WB (Write Back)
  - Not all instructions are active in all phases (except for loads!)
- Controller specifies how to execute instructions
  - Worth thinking about: what new instructions can be added with just most control?

# Your CPU in two parts


- ***Central Processing Unit (CPU):***
  - ***Datapath:*** contains the hardware necessary to perform operations required by the processor
    - Reacts to what the controller tells it! (ie. “I was told to do an add, so I’ll feed these arguments through an adder)
  - ***Control:*** decides what each piece of the datapath should do
    - What operation am I performing? Do I need to get info from memory? Should I write to a register? Which register?
    - Has to make decisions based on the input instruction only!

# Design Principles


- Determining control signals
  - Any time a datapath element has an input that changes behavior, it requires a control signal (e.g. ALU operation, read/write)
  - Any time you need to pass a different input based on the instruction, add a **MUX** with a control signal as the selector (e.g. next PC, ALU input, register to write to)
- Your control signals will change based on your exact datapath
- Your datapath will change based on your ISA
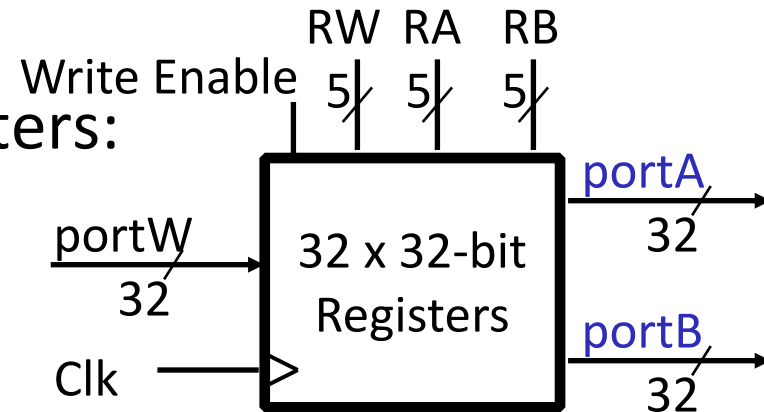
# Storage Element: Register File

- **Register File** consists of 31 registers:
  - Output ports **portA** and **portB**
  - Input port **portW**
- Register selection
  - Place data of register **RA** (number) onto **portA**
  - Place data of register **RB** (number) onto **portB**
  - Store data on **portW** into register **RW** (number) when **Write Enable** is 1
- Clock input (CLK)
  - CLK is passed to all internal registers so they can be written to if they match **RW** and **Write Enable** is 1




# Implementing R-Types

 

## (4) Perform operation


- New hardware: ALU (Arithmetic Logic Unit)
- Abstraction for adders, multipliers, dividers, etc.
- How do we know what operation to execute?
  - Our first control bit! `ALUSel(ect)`

# Adding addi to datapath

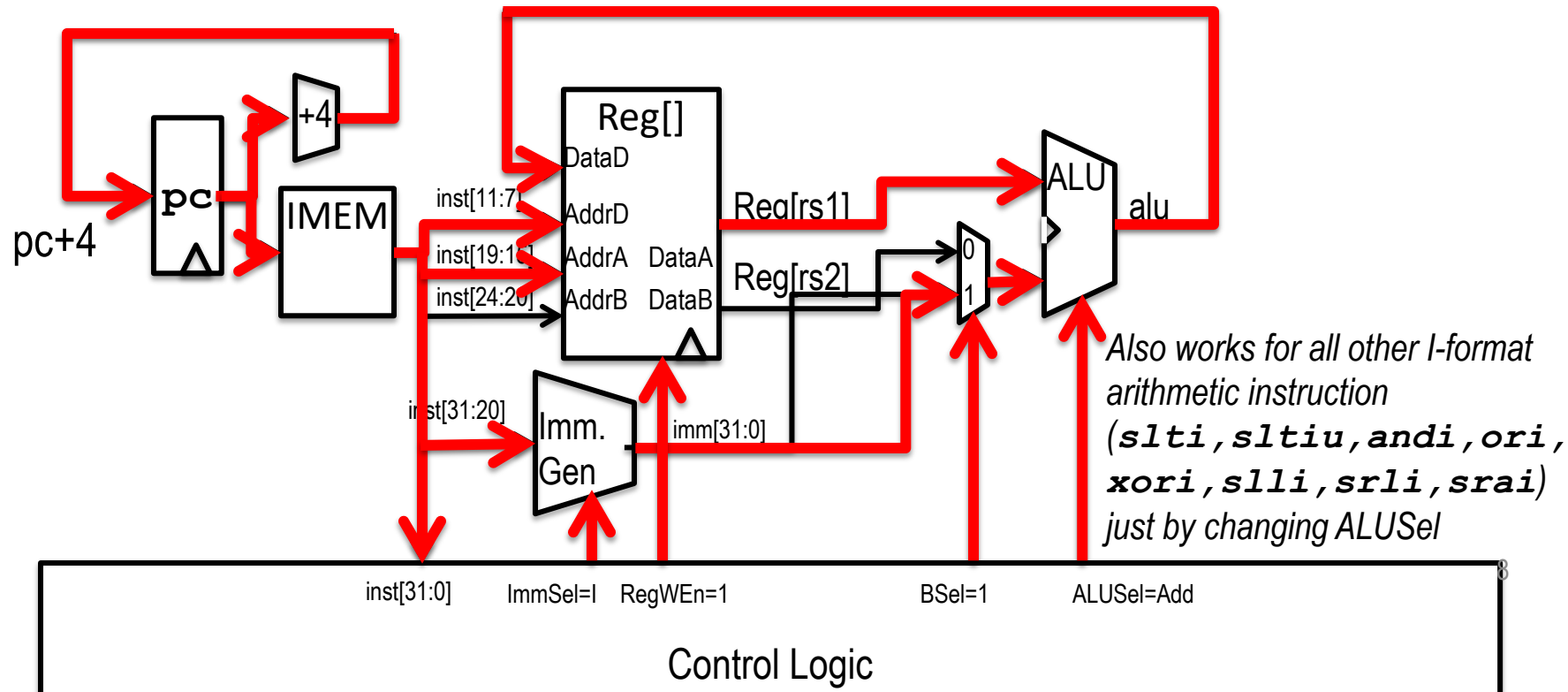




# Adding lw to datapath

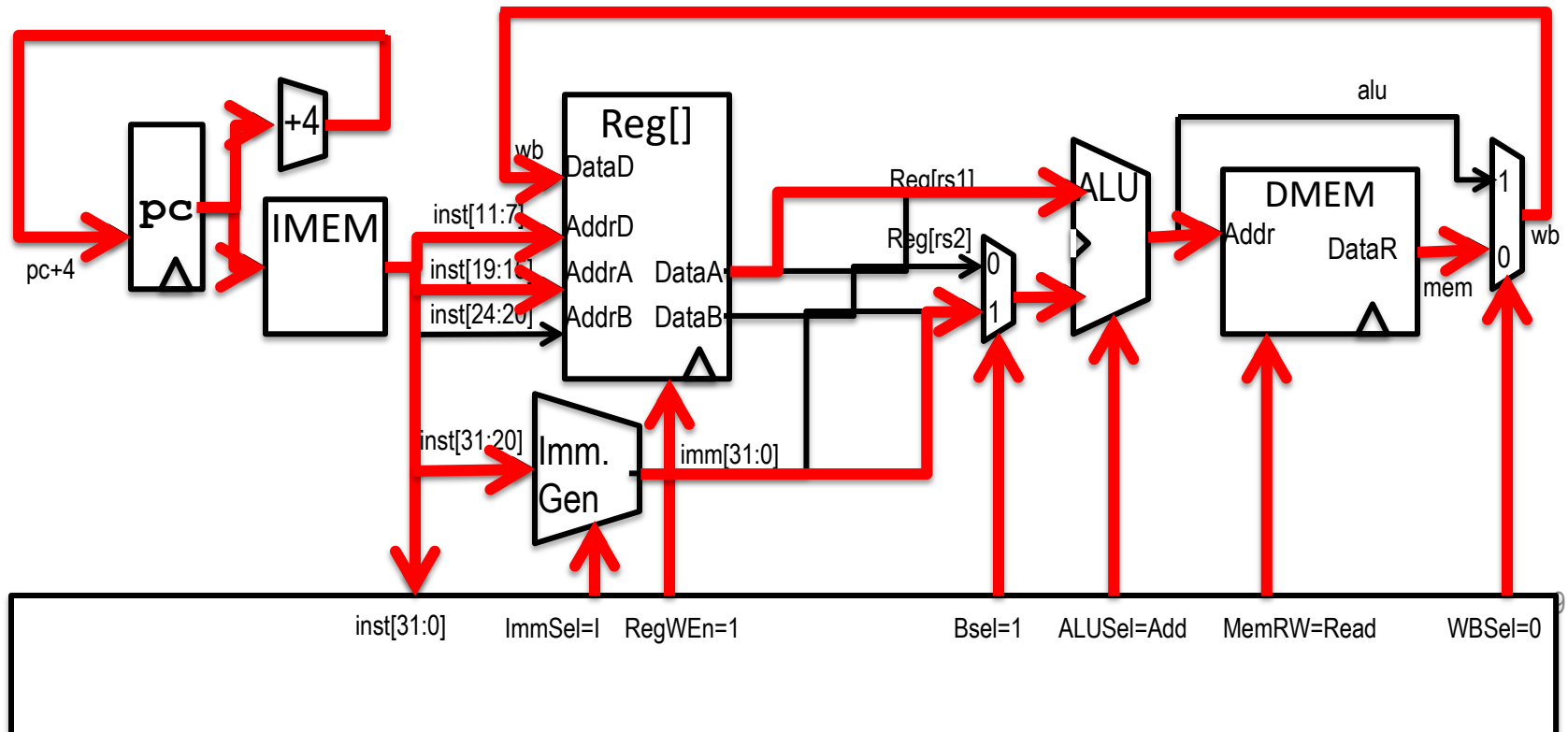

 
# Storage Element: Idealized Memory


- Memory (idealized)
  - One input port: Data In
  - One output port: **Data Out**
- Memory access:
  - Read: Write Enable = 0, data at Address is placed on **Data Out**
  - Write: Write Enable = 1, Data In written to Address
- Clock input (CLK)
  - CLK input is a factor ONLY during write operation
  - During read, behaves as a combinational logic block: Address valid → **Data Out** valid after “access time”




# Current Datapath

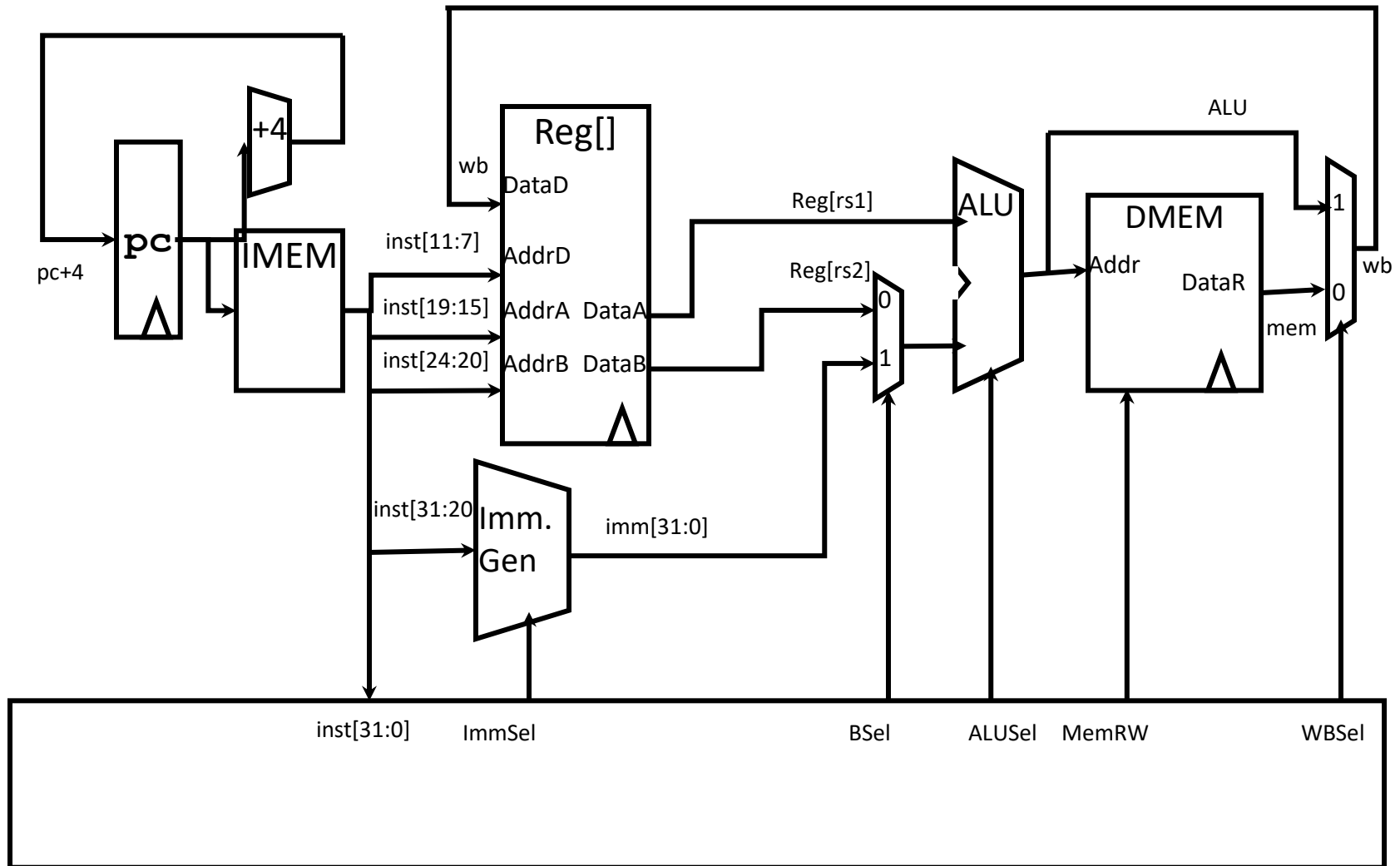


# Adding sw to datapath

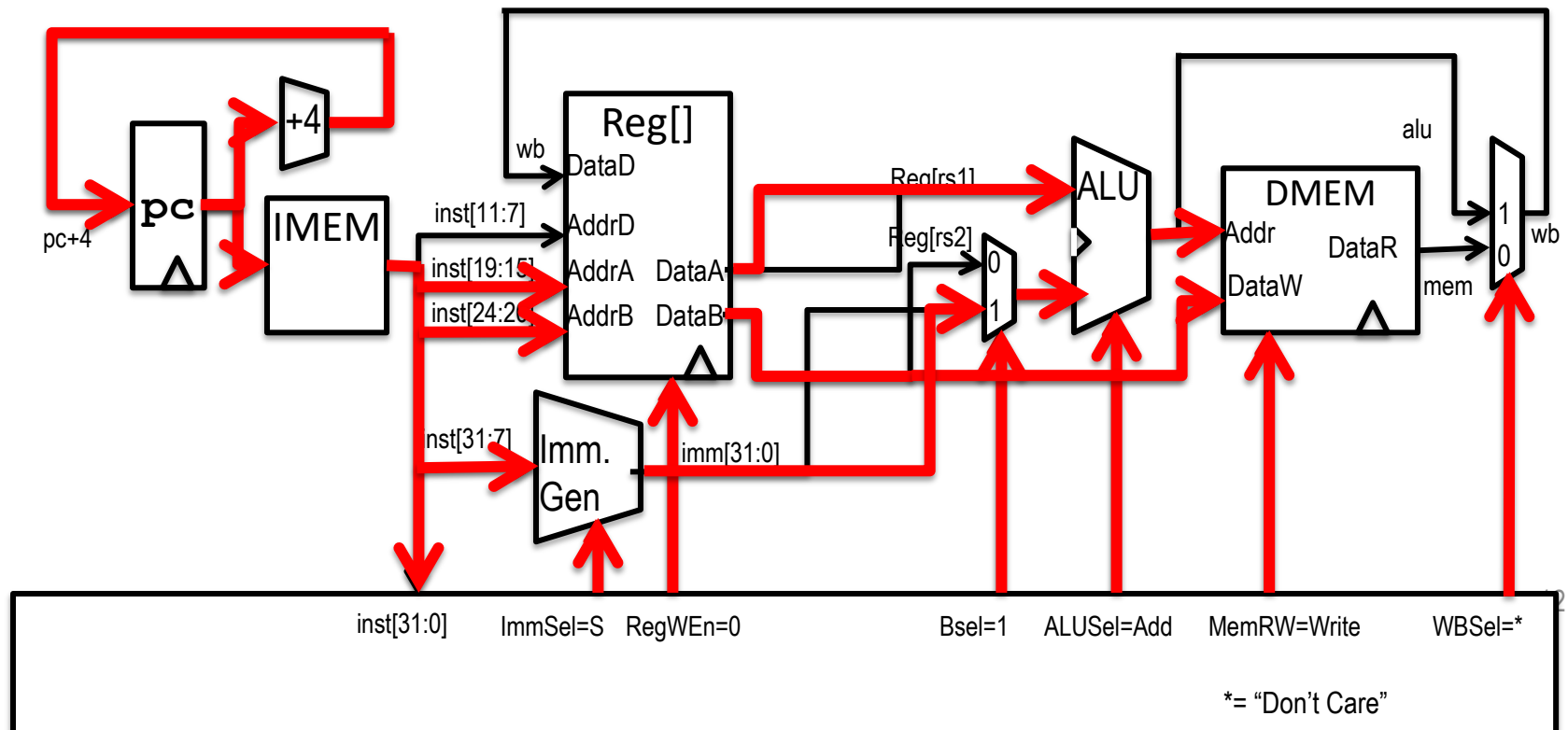


# Adding branches to datapath

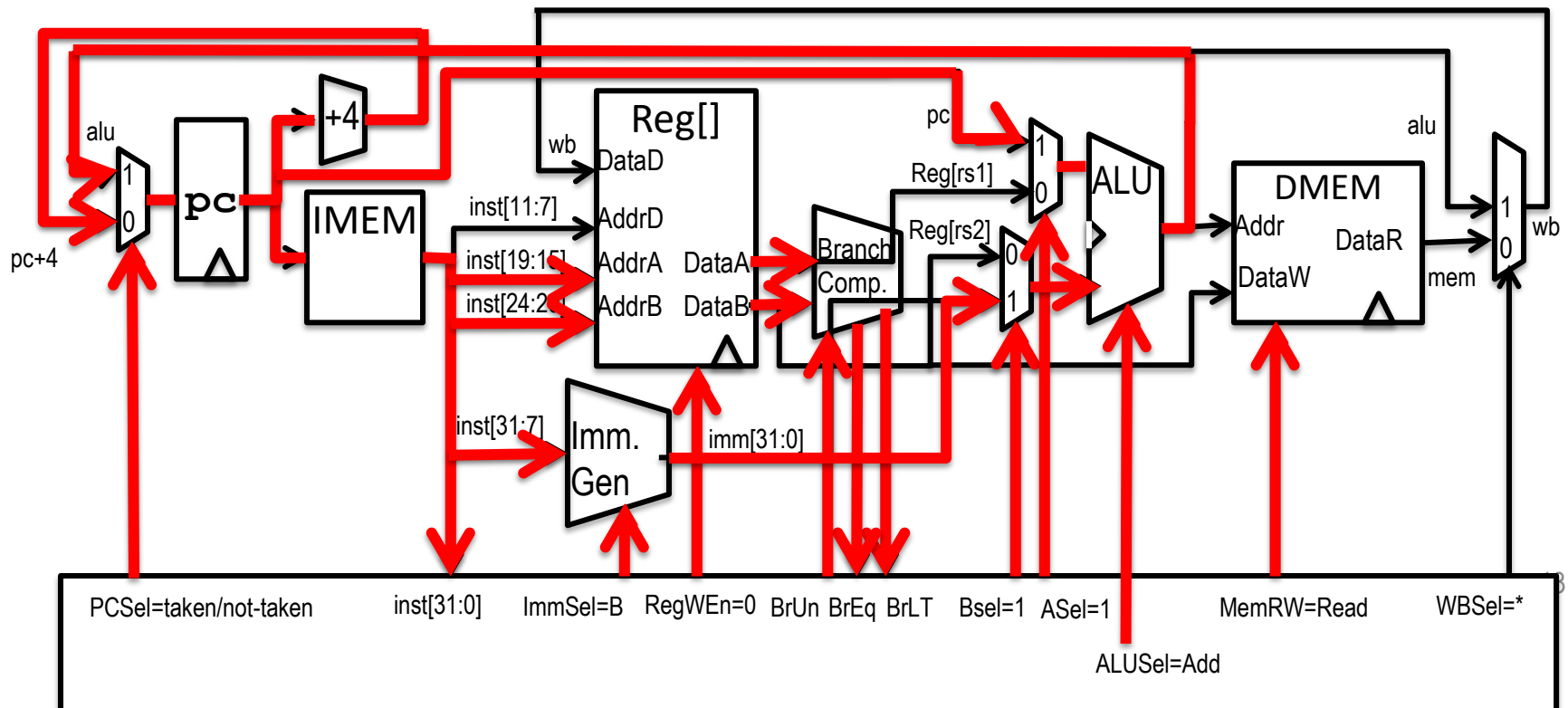


# Adding jalr to datapath

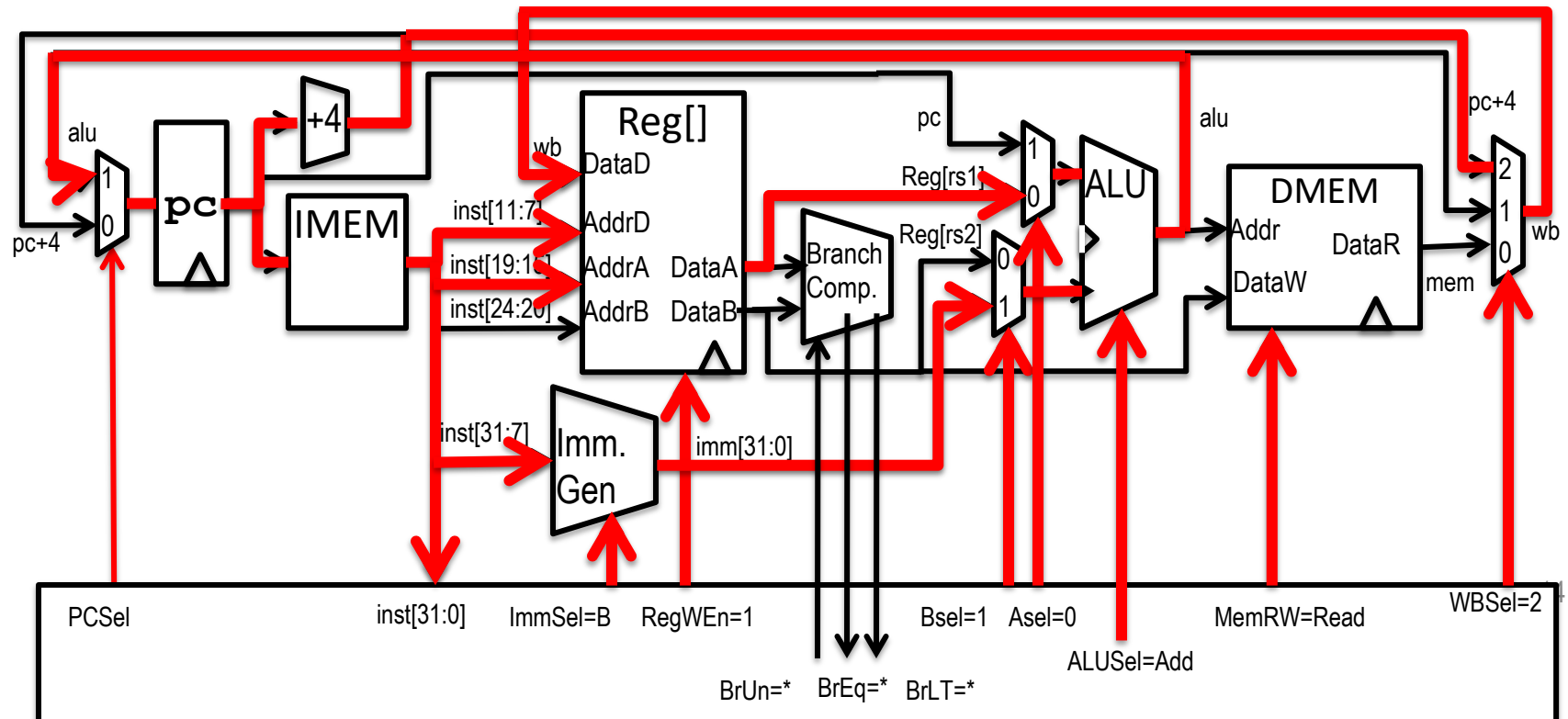

# Adding jal to datapath

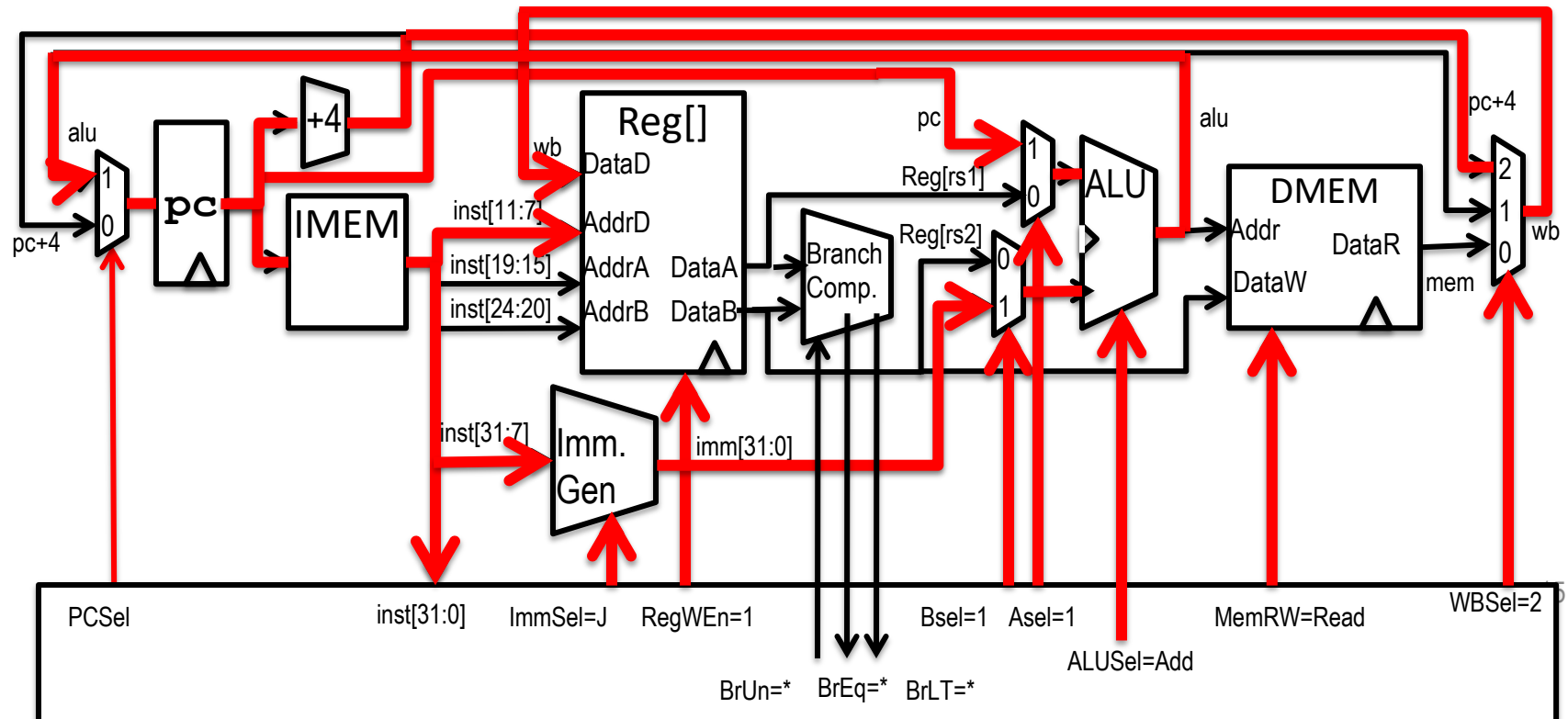

# Implementing lui

 



# Implementing auipc

